

## SIMPLE ELECTRIC CIRCUITS

### Insulator or Conductor? – p3 quiz

1. Materials that electricity can flow through are called \_\_\_\_\_.
  - a. Conductor
  - b. Insulator
2. Materials that stop electricity from flowing are called \_\_\_\_\_.
  - a. Conductor
  - b. Insulator
3. When you placed an object made of metal between the two wires it \_\_\_\_\_ the circuit.
  - a. Closes and completes
  - b. Open and incomplete
4. Paper clip and iron nail are examples of \_\_\_\_\_.
  - a. Insulators
  - b. Conductors
5. Eraser and plastic scale are examples of \_\_\_\_\_.
  - a. Conductors
  - b. Insulators

### ANSWERS

1. A. conductor
2. B. insulator
3. A. closes and completes
4. B. conductors
5. B. insulators